

Quick reference guide to 2-port networks

Variable Assignment

The following principal convention and variables are used for effort and flow assignment.

	linear Mechanical	Mechanical rotation	electrical
e	velocity v	rotational speed ω	voltage v
f	force f	torque T	current i

$$\begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = Z \begin{bmatrix} f_1 \\ f_2 \end{bmatrix} \quad \begin{bmatrix} f_1 \\ f_2 \end{bmatrix} = Y \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} \quad \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = H \begin{bmatrix} f_1 \\ f_2 \end{bmatrix} \quad \begin{bmatrix} f_1 \\ f_2 \end{bmatrix} = G \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} \quad \begin{bmatrix} e_1 \\ f_1 \end{bmatrix} = T \begin{bmatrix} e_2 \\ -f_2 \end{bmatrix}$$

Conversion table

to \ from	Z	Y	H	G	T
Z	$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$	$\begin{bmatrix} y_{22} & -y_{12} \\ \Delta_y & \Delta_y \\ -y_{21} & y_{11} \\ \Delta_y & \Delta_y \end{bmatrix}$	$\begin{bmatrix} \Delta_h & h_{12} \\ h_{22} & h_{22} \\ -h_{21} & h_{22} \\ h_{22} & h_{22} \end{bmatrix}$	$\begin{bmatrix} 1 & -g_{12} \\ g_{11} & g_{11} \\ g_{21} & \Delta_g \\ g_{11} & g_{11} \end{bmatrix}$	$\begin{bmatrix} t_{11} & \Delta_t \\ t_{21} & t_{21} \\ 1 & t_{22} \\ t_{21} & t_{21} \end{bmatrix}$
Y	$\begin{bmatrix} z_{22} & -z_{12} \\ \Delta_z & \Delta_z \\ -z_{21} & z_{11} \\ \Delta_z & \Delta_z \end{bmatrix}$	$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$	$\begin{bmatrix} 1 & -h_{12} \\ h_{11} & h_{11} \\ h_{21} & \Delta_h \\ h_{11} & h_{11} \end{bmatrix}$	$\begin{bmatrix} \Delta_g & g_{12} \\ g_{22} & g_{22} \\ -g_{21} & 1 \\ g_{22} & g_{22} \end{bmatrix}$	$\begin{bmatrix} t_{22} & -\Delta_t \\ t_{12} & t_{22} \\ -1 & t_{11} \\ t_{12} & t_{12} \end{bmatrix}$
H	$\begin{bmatrix} \Delta_z & z_{12} \\ z_{22} & z_{22} \\ -z_{21} & 1 \\ z_{22} & z_{22} \end{bmatrix}$	$\begin{bmatrix} 1 & -y_{12} \\ y_{11} & y_{11} \\ y_{21} & \Delta_y \\ y_{11} & y_{11} \end{bmatrix}$	$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$	$\begin{bmatrix} g_{22} & -g_{12} \\ \Delta_g & \Delta_g \\ -g_{21} & g_{11} \\ \Delta_g & \Delta_g \end{bmatrix}$	$\begin{bmatrix} t_{12} & \Delta_t \\ t_{22} & t_{22} \\ -1 & t_{21} \\ t_{22} & t_{22} \end{bmatrix}$
G	$\begin{bmatrix} 1 & -z_{12} \\ z_{11} & z_{11} \\ z_{21} & \Delta_z \\ z_{11} & z_{11} \end{bmatrix}$	$\begin{bmatrix} \Delta_y & y_{12} \\ y_{22} & y_{22} \\ -y_{21} & 1 \\ y_{22} & y_{22} \end{bmatrix}$	$\begin{bmatrix} h_{22} & -h_{12} \\ \Delta_h & \Delta_h \\ -h_{21} & h_{11} \\ \Delta_h & \Delta_h \end{bmatrix}$	$\begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix}$	$\begin{bmatrix} t_{21} & -\Delta_t \\ t_{11} & t_{11} \\ 1 & t_{12} \\ t_{11} & t_{11} \end{bmatrix}$
T	$\begin{bmatrix} z_{11} & \Delta_z \\ z_{21} & z_{21} \\ 1 & z_{22} \\ z_{21} & z_{21} \end{bmatrix}$	$\begin{bmatrix} -y_{22} & -1 \\ y_{21} & y_{21} \\ -\Delta_y & -y_{11} \\ y_{21} & y_{21} \end{bmatrix}$	$\begin{bmatrix} -\Delta_h & -h_{11} \\ h_{21} & h_{21} \\ -h_{22} & -1 \\ h_{21} & h_{21} \end{bmatrix}$	$\begin{bmatrix} 1 & g_{22} \\ g_{21} & g_{21} \\ g_{11} & \Delta_g \\ g_{21} & g_{21} \end{bmatrix}$	$\begin{bmatrix} t_{11} & t_{12} \\ t_{21} & t_{22} \end{bmatrix}$

Combining two-ports

If the two ports are not cascaded then add. Series implies common flow, parallel implies common effort.

Left port	right port	add when in :-
Series	series	Impedance (Z) form
Parallel	parallel	Admittance (Y) form
Series	parallel	Hybrid-H form
Parallel	series	Hybrid-G form

- Series implies that flow is conserved at the connected ports
- parallel implies that effort is conserved at the connected ports

Alternatively and equivalently

port2 \ port1	e	f
e	Y	H
f	G	Z

If the two port networks are in a cascade then they need to be in transmission form T and the combination is then done by matrix multiplication.

Transfer functions (gain table)

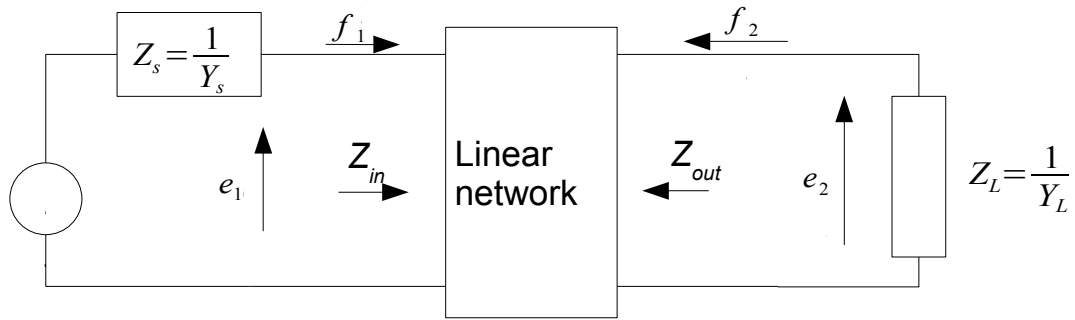


Figure 1. Termination of a generic 2-port network

		Z	Y	G	H	T
Zin	$Z_i = \frac{e_1}{f_1}$	$\frac{\Delta_z + z_{11}Z_L}{z_{22} + Z_L}$	$\frac{y_{22} + Y_L}{\Delta_y + y_{11}Y_L}$	$\frac{g_{22} + Z_L}{\Delta_g + g_{22}Z_L}$	$\frac{\Delta_h + h_{11}Y_L}{h_{22} + Y_L}$	$\frac{t_{11}Z_L + t_{12}}{t_{21}Z_L + t_{22}}$
Zout	$Z_o = \frac{e_2}{f_2}$	$\frac{\Delta_z + z_{22}Z_s}{z_{11} + Z_s}$	$\frac{y_{11} + Y_s}{\Delta_y + y_{22}Y_s}$	$\frac{\Delta_g + g_{22}Y_s}{g_{11} + Y_s}$	$\frac{h_{11} + Z_s}{\Delta_h + h_{22}Z_s}$	$\frac{t_{22}Z_s + t_{12}}{t_{21}Z_s + t_{11}}$
Flow gain	$A_f = -\frac{f_2}{f_1}$	$\frac{z_{21}}{z_{22} + Z_L}$	$\frac{-y_{21}Y_L}{\Delta_y + y_{11}Y_L}$	$\frac{g_{21}}{\Delta_g + g_{11}Z_L}$	$\frac{-h_{21}Y_L}{h_{22} + Y_L}$	$\frac{1}{t_{22} + t_{21}Z_L}$
Effort gain	$A_e = \frac{e_2}{e_1}$	$\frac{z_{21}Z_L}{\Delta_z + z_{11}Z_L}$	$\frac{-y_{21}}{y_{22} + Y_L}$	$\frac{g_{21}Z_L}{g_{22} + Z_L}$	$\frac{-h_{21}}{\Delta_h + h_{11}Y_L}$	$\frac{Z_L}{t_{12} + t_{11}Z_L}$
effort to flow gain	$A_{fe} = \frac{e_2}{f_1}$				$\frac{-h_{21}}{h_{22} + Y_L}$	$\frac{Z_L}{t_{22} + t_{21}Z_L}$
effort to flow gain	$A_{ef} = -\frac{f_2}{e_1}$				$\frac{-h_{21}}{\Delta_h Z_L + h_{11}}$	$\frac{1}{t_{12} + t_{11}Z_L}$

Note that $A_{fe} = \frac{e_2}{f_1} = A_f Z_L$, and $A_{ef} = -\frac{f_2}{e_1} = A_e Y_L$. Also $Z_i = Z_L \frac{A_f}{A_e}$.